



TUTORIAL: All-GaN GaN-ICs in the IMEC's GaN-on-SOI technology


STEFAN DECOUTERE AUG' 2019

WHAT IS THIS TUTORIAL ABOUT ?

INTRODUCTION

GaN discrete components

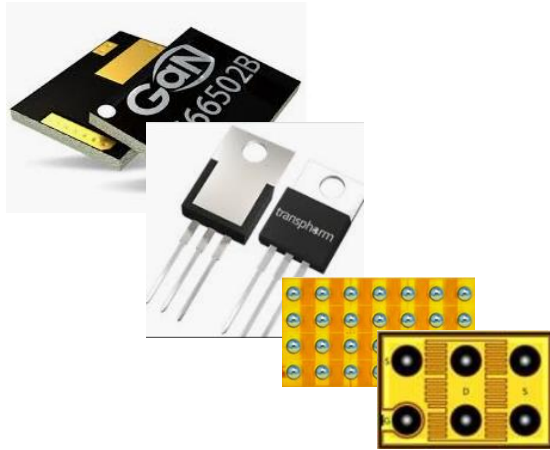- Dominate the GaN market today
- Off-the-shelf components or customized designs through foundry



Monolithic integration

- To unlock full potential of fast switching GaN technology:
 - Reduction of parasitics between driver and power device
 - Reduction of parasitics on switching node of half-bridge
- For those applications where it makes sense, both performance wise as cost-wise

Technological problems to solve

- Back-gating effects in half-bridges
- Low-voltage control and diagnostics circuits monolithically integrated with high-voltage power devices
- Suite of passive components


Circuit design problems to solve

- Design of gate driver without complementary devices
- Level shifting for high-side driver/switch
- Logic gates / Analog sub-circuits without complementary devices


WHAT IS THIS TUTORIAL ABOUT ?

FROM DISCRETE COMPONENTS TO GaN-ICs


3 dies

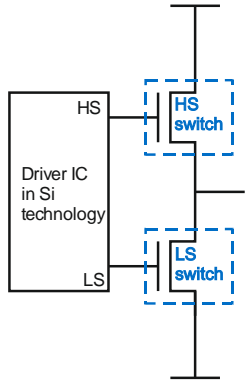


2 dies

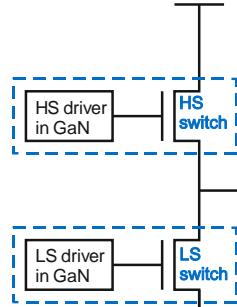

2 dies

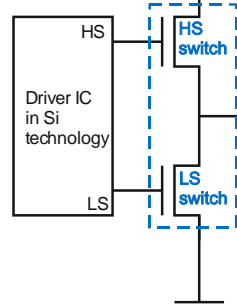


1 die

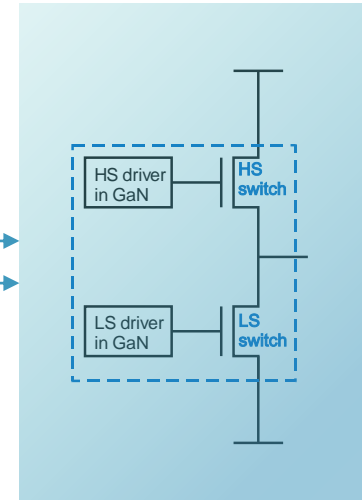

THIS IS WHAT THIS TUTORIAL IS ABOUT !

WHAT IS THIS TUTORIAL ABOUT ?

FROM DISCRETE COMPONENTS TO GaN-ICs

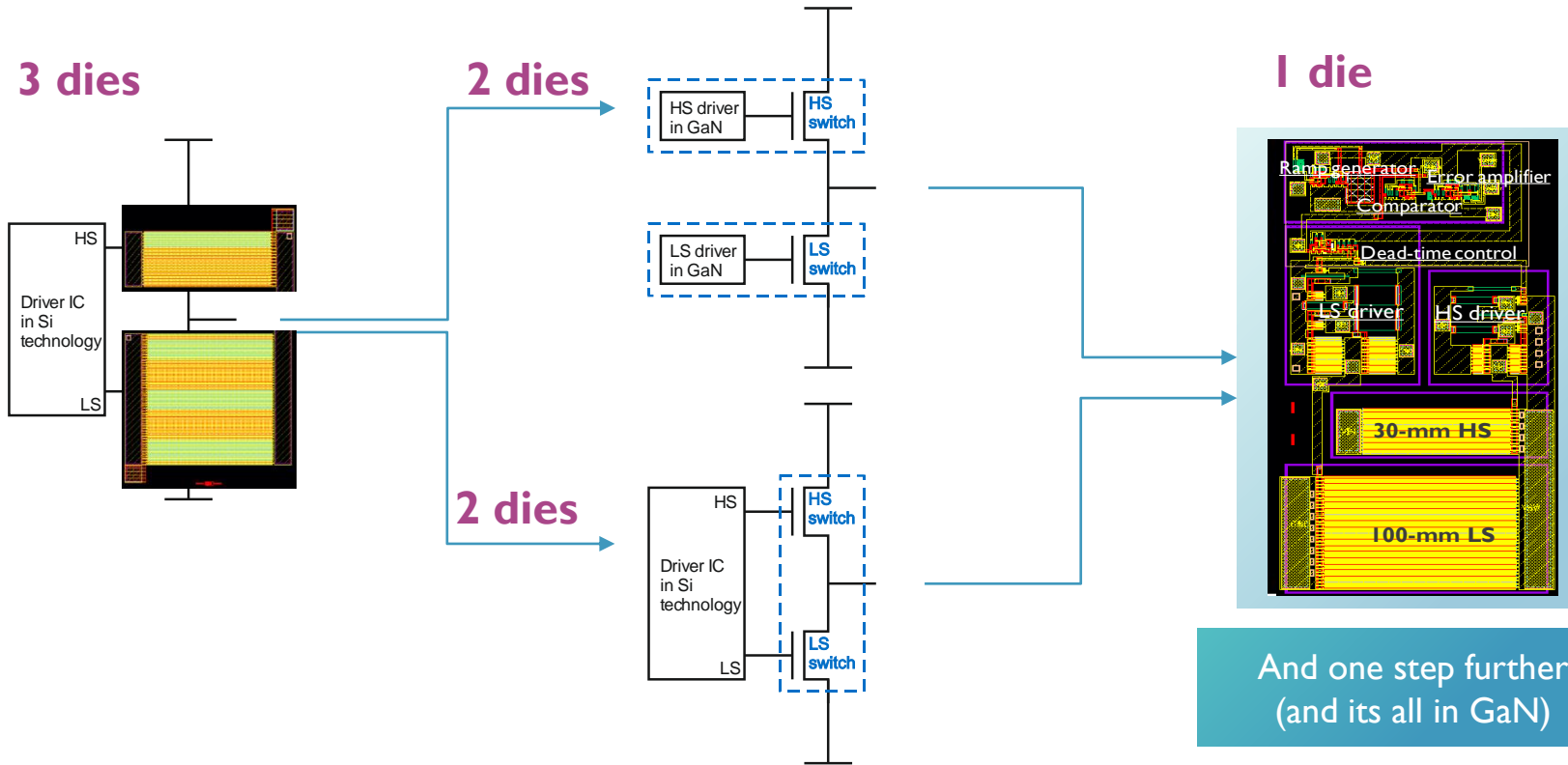

BACK-GATING EFFECT IN HALF-BRIDGES

KNOWN EFFECT IN CMOS

BODY EFFECT

Change in threshold voltage ... When $V_{SB} \neq 0$ Volt


Body effect

The *body effect* is the change in the threshold voltage by an amount approximately equal to the change in the source-bulk voltage, V_{SB} , because the body influences the threshold voltage (when it is not tied to the source). It can be thought of as a second gate, and is sometimes referred to as the *back gate*, and accordingly the body effect is sometimes called the *back-gate effect*.^[1]

For an enhancement-mode nMOS MOSFET, the body effect upon threshold voltage is computed according to the Shichman–Hodges model,^[2] which is accurate for older process nodes,^[clarification needed] using the following equation:


$$V_{TN} = V_{TO} + \gamma \left(\sqrt{|V_{SB} + 2\phi_F|} - \sqrt{|2\phi_F|} \right)$$

where V_{TN} is the threshold voltage when substrate bias is present, V_{SB} is the source-to-body substrate bias, $2\phi_F$ is the surface potential, and V_{TO} is threshold voltage for zero substrate bias, $\gamma = (t_{ox}/\epsilon_{ox}) \sqrt{2q\epsilon_{Si}N_A}$ is the body effect parameter, t_{ox} is oxide thickness, ϵ_{ox} is oxide permittivity, ϵ_{Si} is the permittivity of silicon, N_A is a doping concentration, q is elementary charge.

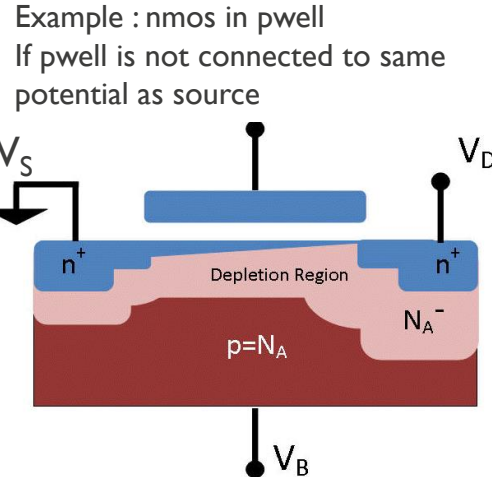


BACK-GATING EFFECT IN P-GAN HEMT ?

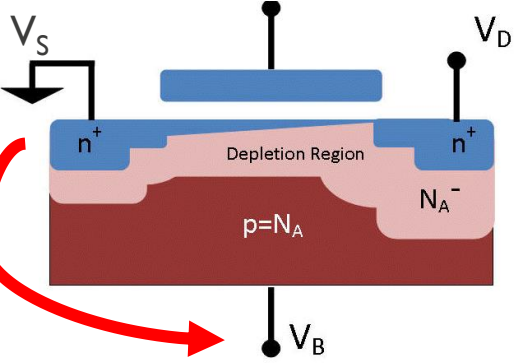
Example : nmos in pwell
If pwell is not connected to same potential as source



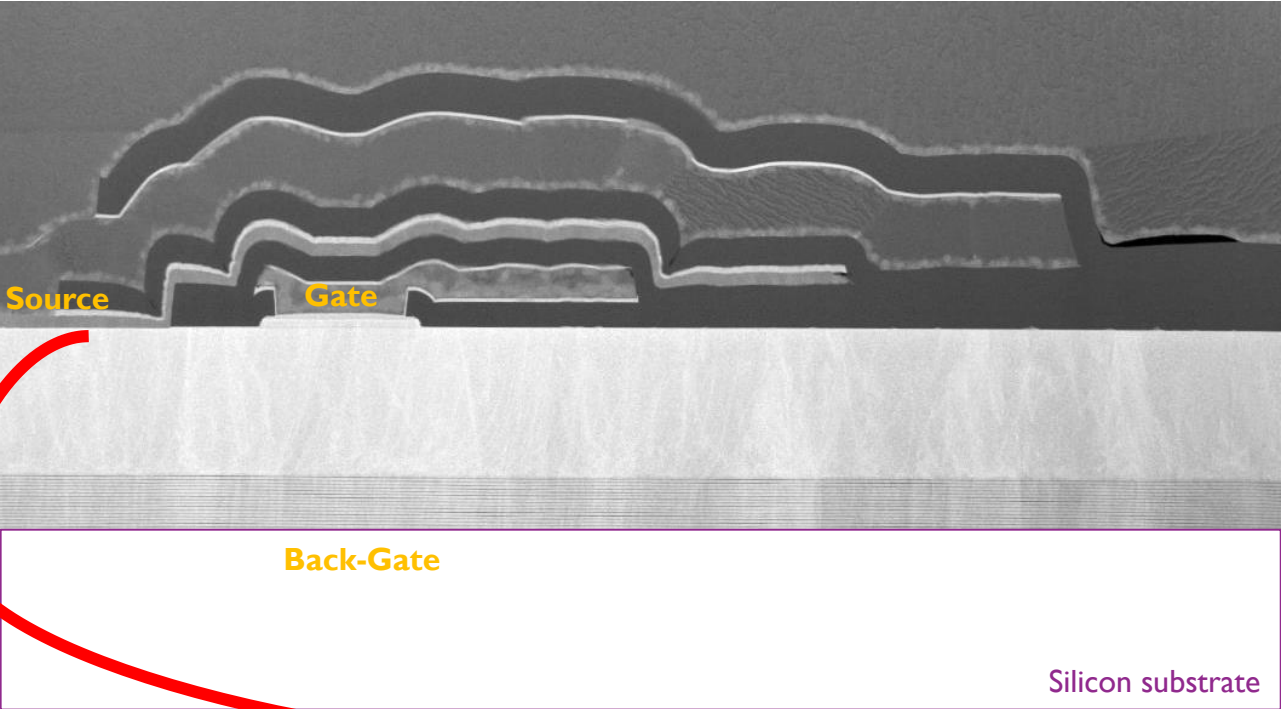
Example : p-GaN HEMT on Silicon substrate



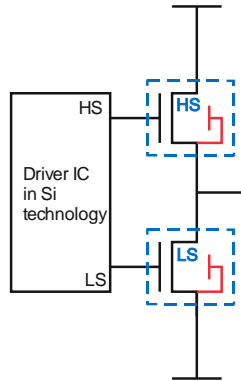WHY IS IT IMPORTANT FOR MONOLITHIC INTEGRATION OF HALF-BRIDGES ?



Discrete devices : $V_{SB} = 0$ Volt

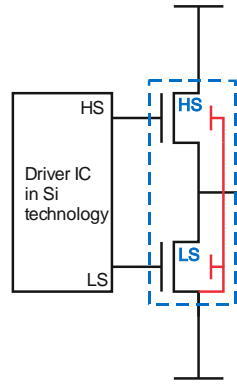

Monolithic half-bridge : $V_{SB} \neq 0$ Volt

Loss in substrate ?

Back-gating in HS switch ?

Example for $V_{in} = 200$ Volt.

When HS switch is ON, and
LS switch is OFF :

$$V_{S_LS} = 0 \text{ Volt}$$


$$V_{SB_LS} = 0 \text{ Volt}$$

$$V_{S_HS} \sim 199 \text{ Volt}$$

- Current in substrate
- Disconnect substrate from Source_HS, then $V_{SB} = 199$ Volt




PROPOSED SOLUTION

GaN-on-SOI WITH DEEP TRENCH ISOLATION

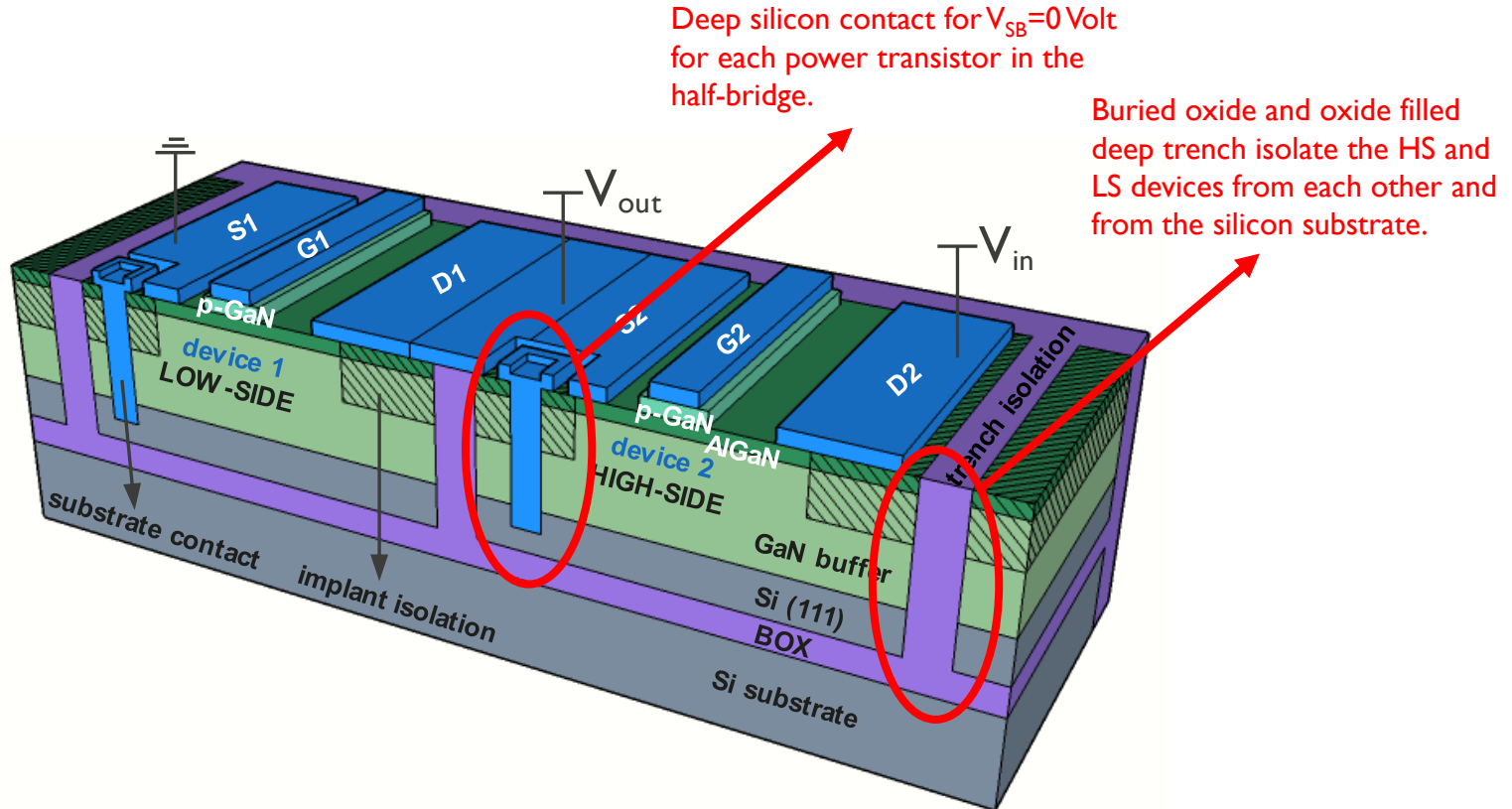

ELECTRICAL MEASUREMENT OF GaN-on-SOI




BACKGATING EFFECT

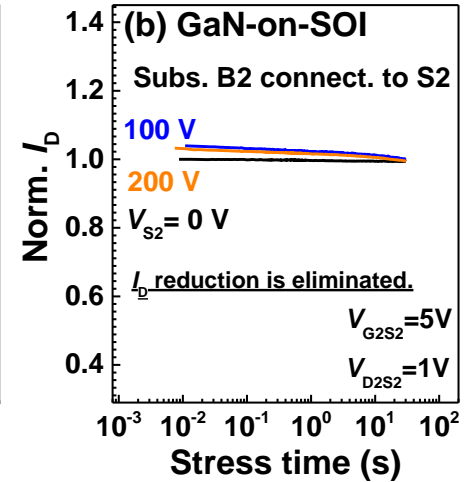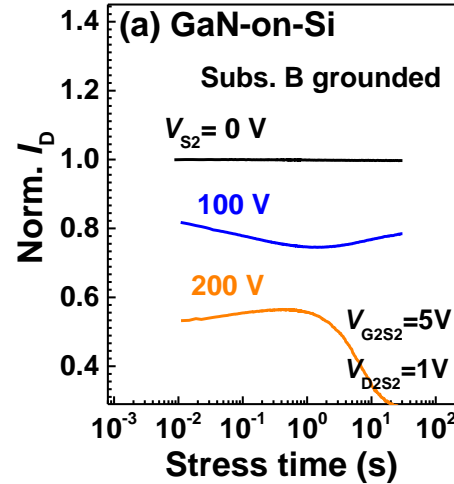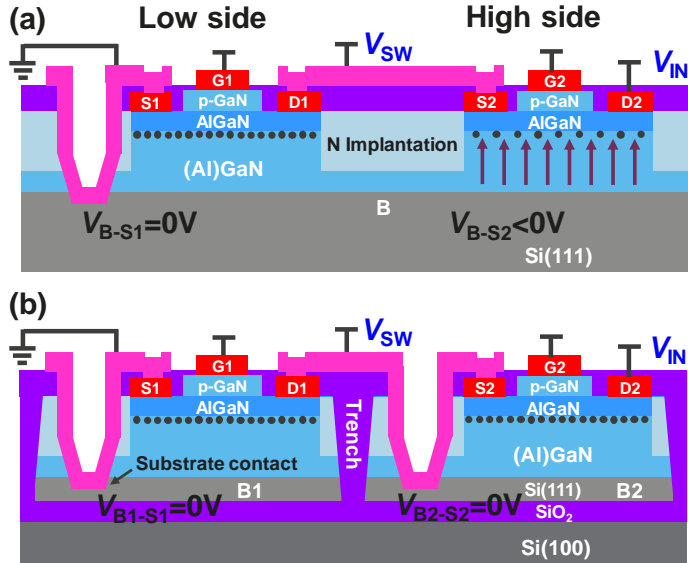

- The backgating effect can be fully **eliminated** by connecting the source terminals to their respective Si(111) device layer.

ELECTRICAL MEASUREMENT OF GaN-on-SOI




BACKGATING EFFECT

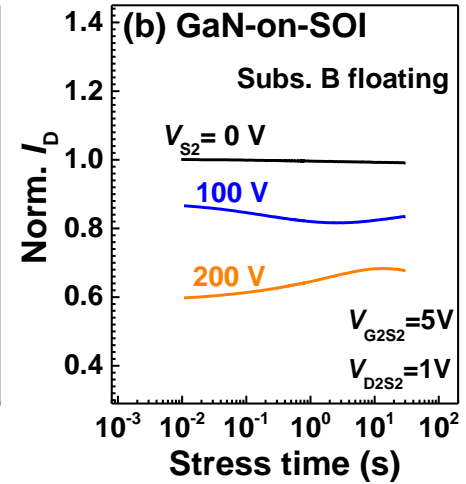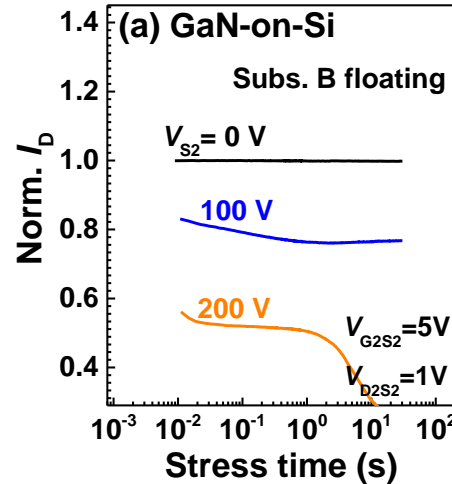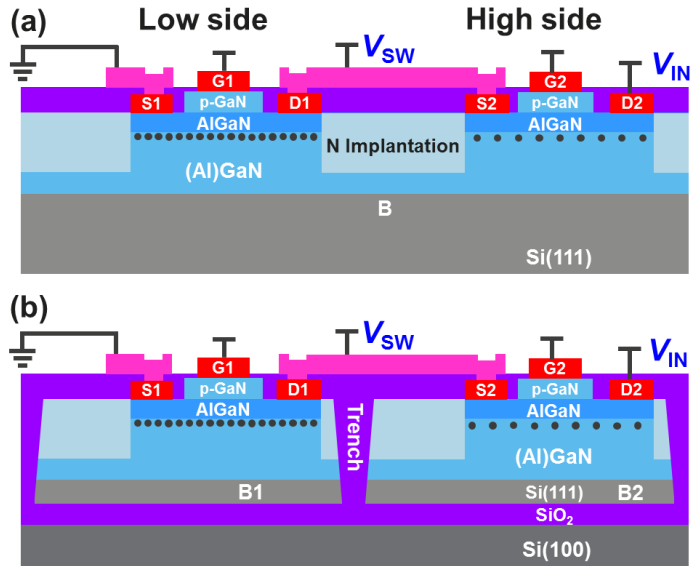

- The backgating effect **cannot** be removed by simply **floating** the Si(111) device layer;
- The substrate contact is **indispensable**.

ELECTRICAL CHARACTERISTICS P-GAN POWER HEMT AND ISOLATION



BUFFER CHARACTERISTICS

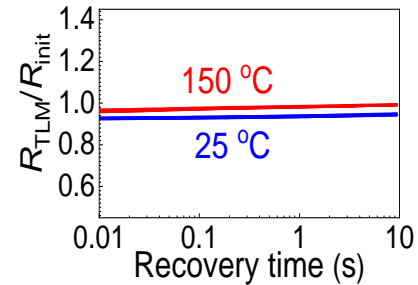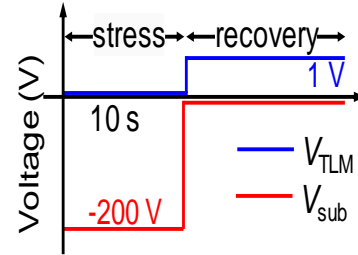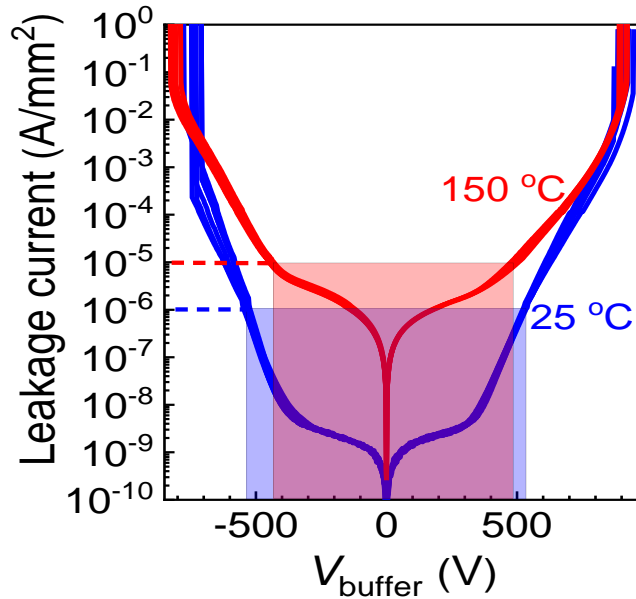

Buffer leakage in spec over temperature range and voltage range. Stress and recovery measurements on the buffer using a 2DEG resistor shows that the buffer is low in dispersion over temperature range. (Trapping effects in buffer under control)


ISOLATION

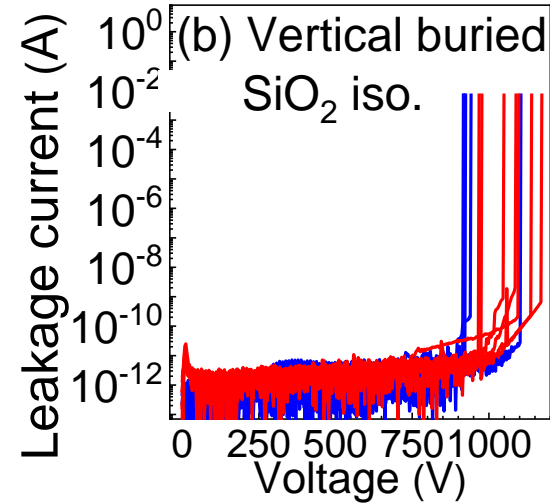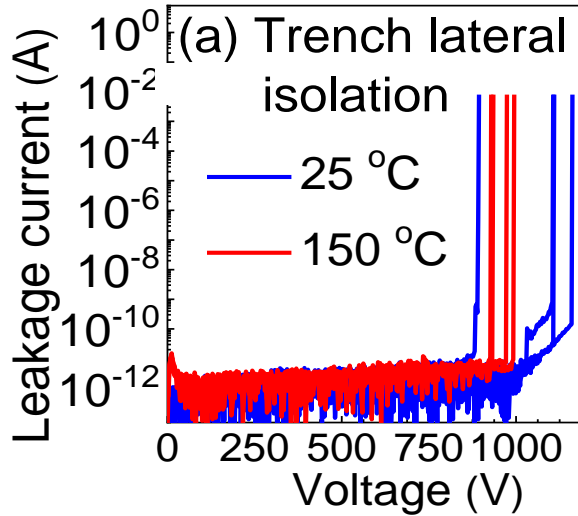HIGH BREAKDOWN VOLTAGE FOR LATERAL AND VERTICAL ISOLATION OF HEMT_s



P-GAN HEMT KEY CHARACTERISTICS


HEMT with $W_{EF} = 40\text{mm}$

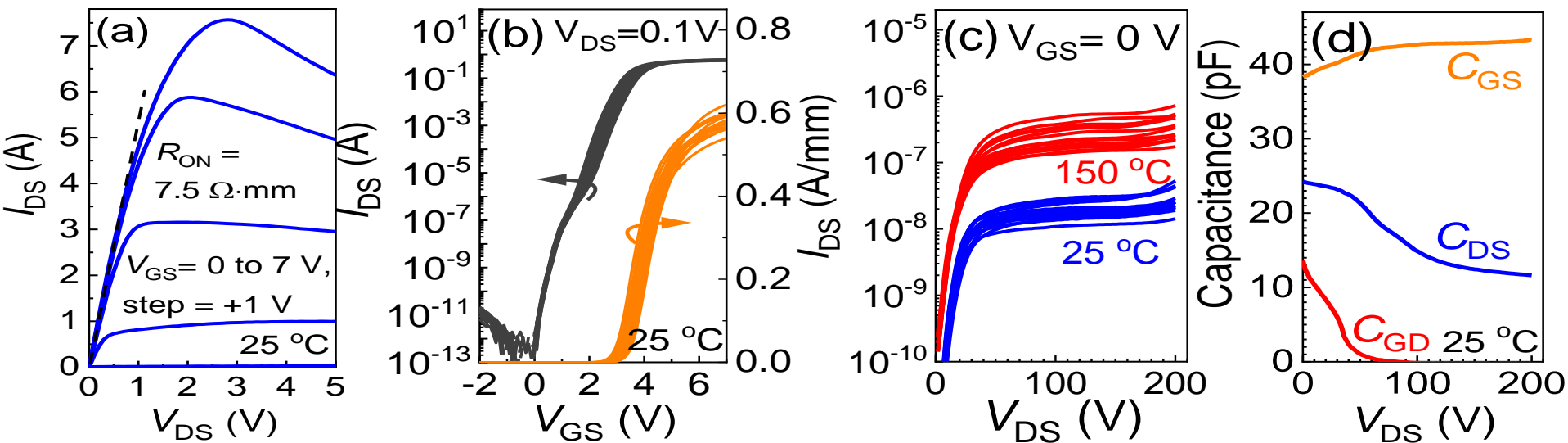


Power devices are modeled using the MVSG model, supported by the Compact Modeling Coalition

DEVICE DISPERSION

DYNAMIC R_{ON}

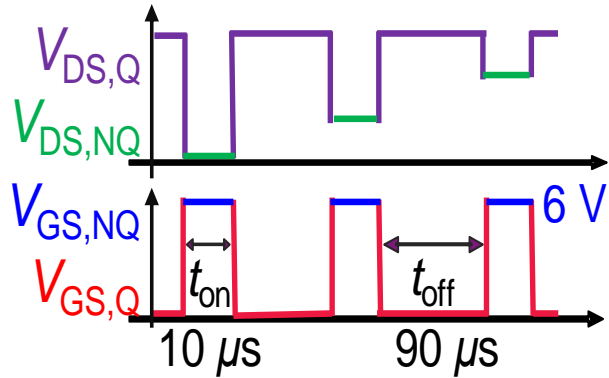

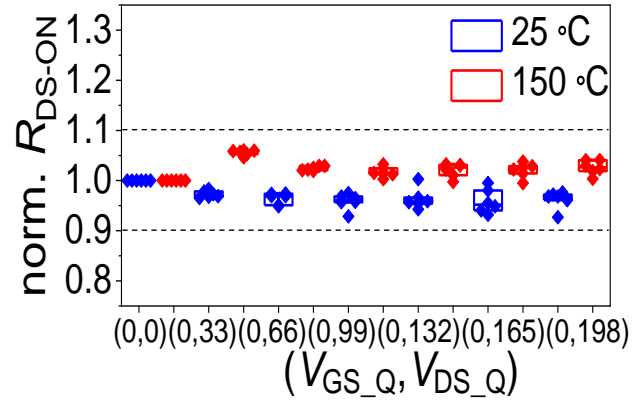Pulse conditions for measurement of the dynamic R_{DS_ON}




Normalized dynamic R_{DS_ON} as a function of the quiescent voltage. Very low dispersion is observed.

INTEGRATED PASSIVE COMPONENTS (FREE COMPONENTS)

INTEGRATED PASSIVE COMPONENTS THAT COME FREE WITH THE TECHNOLOGY

High-ohmic Resistor

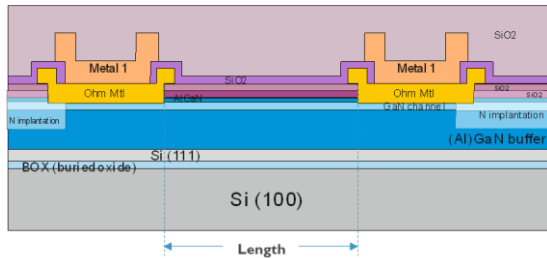Resistor using the 2-dimensional electron gas. $600 \Omega/\square$




Spice model including :

- Linear and quadratic voltage linearity coefficients
- Linear and quadratic temperature coefficients

Low Ohmic resistor

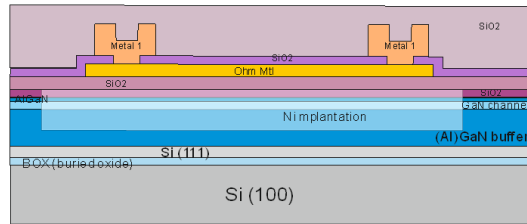Resistor using the metal layer of the ohmic contacts. $1.7 \Omega/\square$




Spice model including :

- Linear voltage linearity coefficient
- Linear and quadratic temperature coefficients

MIM capacitor

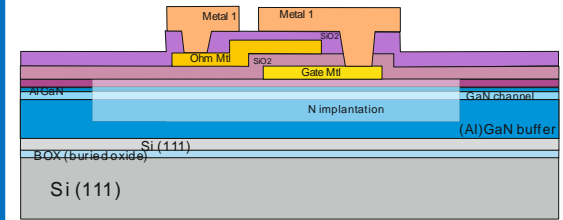Back-end capacitor using the metal layers for the ohmic contacts, gate metal and metal 1. $0.3 \text{ fF}/\mu\text{m}^2$







Layout recommendation :

- Electrode in Ohmic metal has large series resistance
- Use stripe geometry capacitor unit cells for Rs reduction



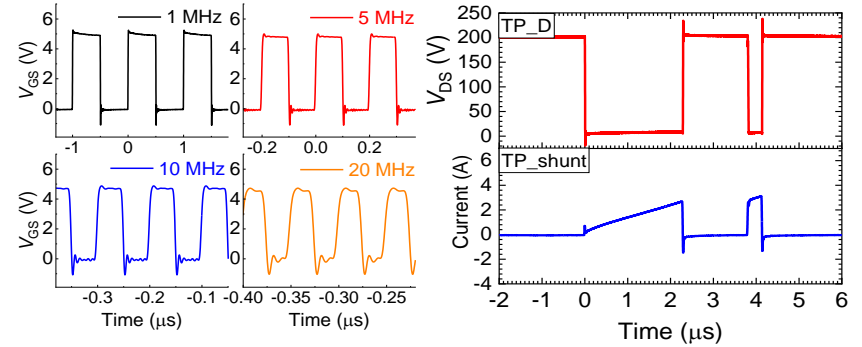
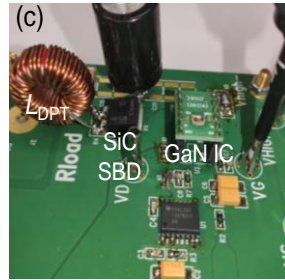
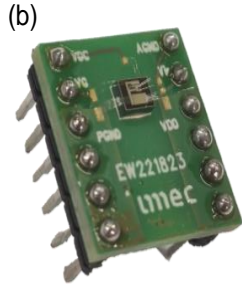
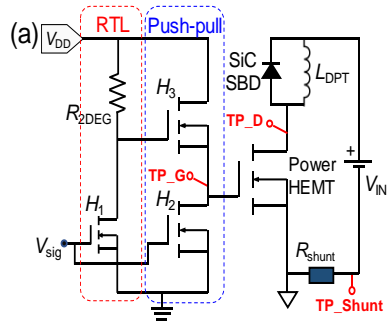
EXAMPLES : P-GAN HEMTS WITH INTEGRATED DRIVERS

P-GAN HEMT WITH INTEGRATED DRIVER DEMONSTRATION



HALF-BRIDGE WITH INTEGRATED DRIVERS

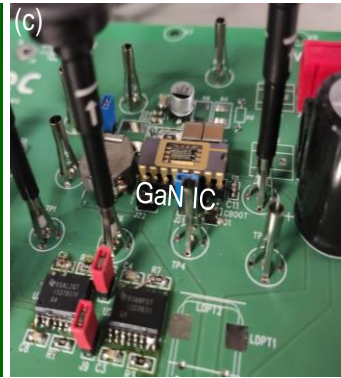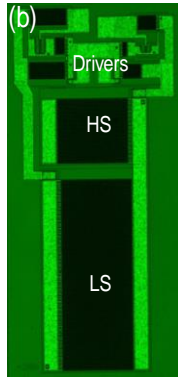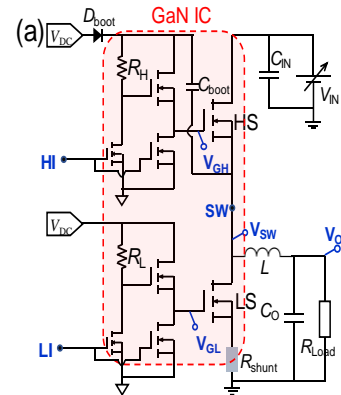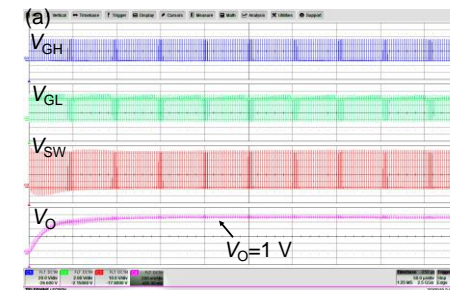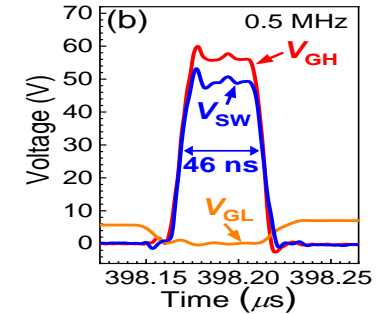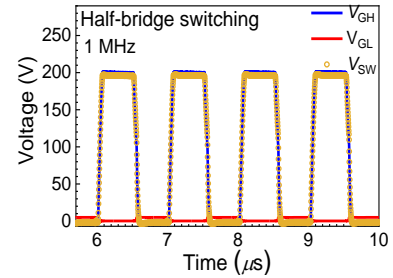DEMONSTRATION IN 48 TO 1 VOLT BUCK CONVERTER












EXAMPLES : LOGIC GATES

LOGIC FUNCTIONS IN A GaN POWER TECHNOLOGY

RTL : RESISTOR – TRANSISTOR LOGIC

Using the 2DEG resistor and a low voltage GaN HEMT, basic logic functions can be designed in RTL (Resistor-Transistor Logic):

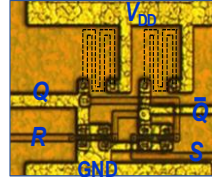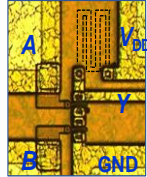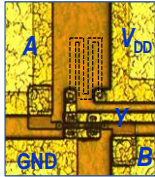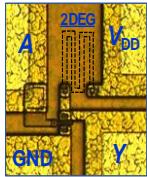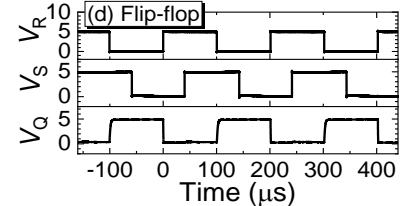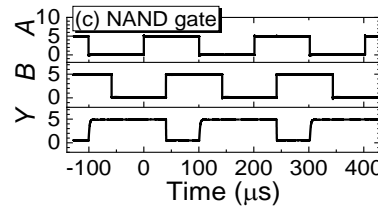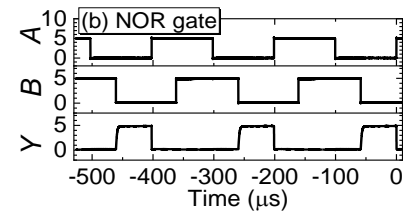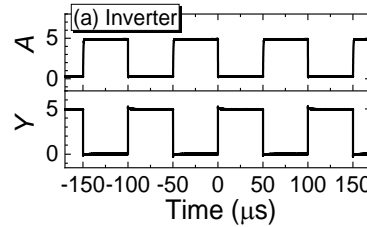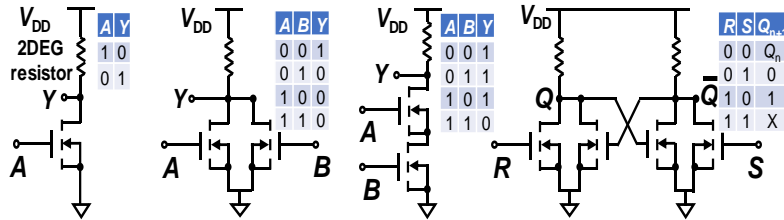- The low voltage GaN HEMT is designed with small effective gate width (e.g. $6\mu\text{m}$) and $L_{\text{GD}} = 1.5\mu\text{m}$.
- Threshold voltage is approximately the same as for the power device.



(a) Inverter

(b) NOR



(c) NAND

(d) Flip-flop


EXAMPLES :ANALOG FUNCTIONS / PROTECTION CIRCUITS / ...

ANALOG BLOCK DESIGN USING TRANSISTORS/RESISTORS/CAPACITORS

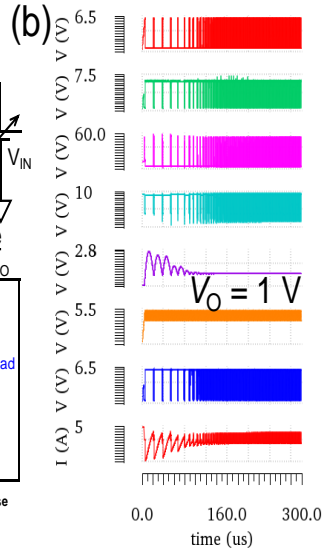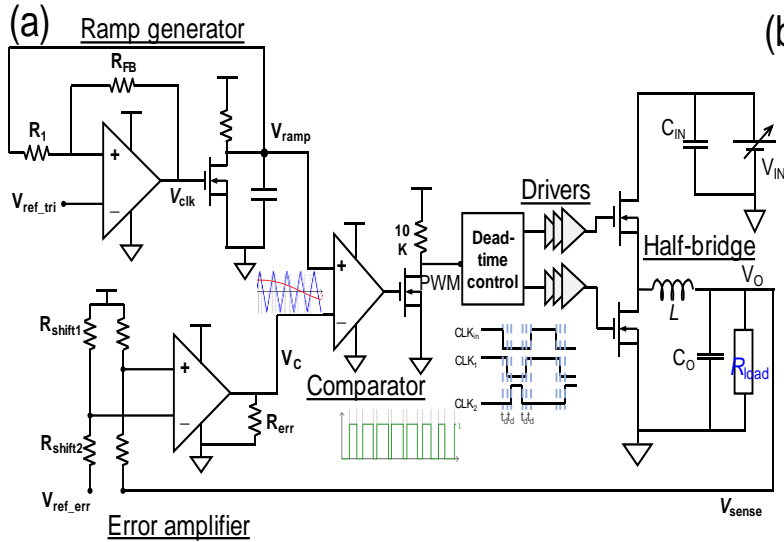Example 1 : 48 to 1 Volt (monolithic) buck converter



(Simulation result)

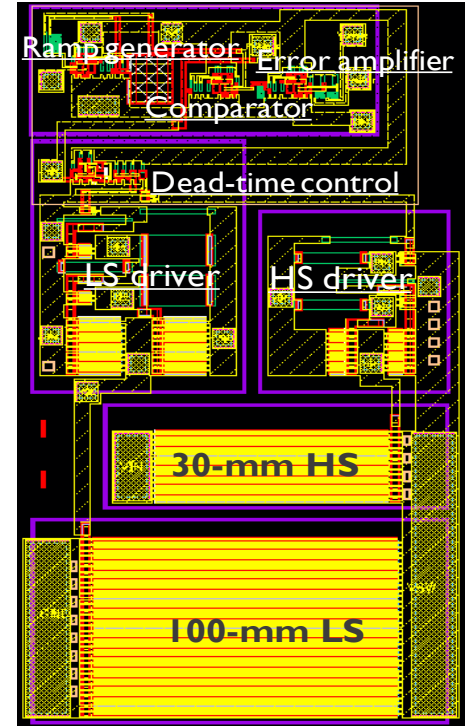

DIAGNOSTIC AND PROTECTION CIRCUITS

EXAMPLES




Undervoltage lock-out

Over-Temperature protection

Over-current protection

All – GaN


... Monolithically integrated !

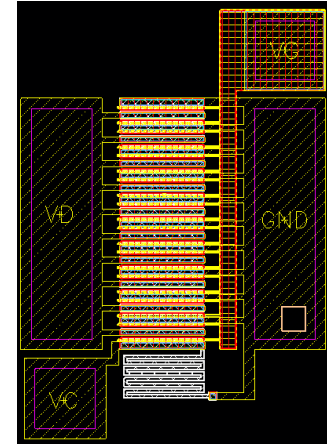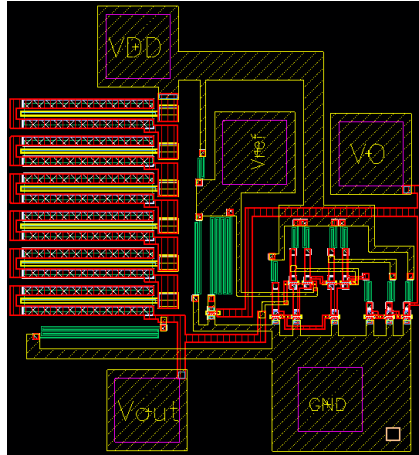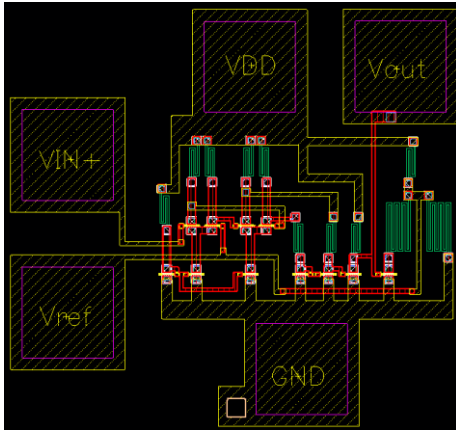

HOW TO GET ACCESS TO THIS GaN-IC TECHNOLOGY ? GaN-IC PROTOTYPING AND VOLUME PRODUCTION

TECHNOLOGY ACCESS (PROTOTYPING)

- MULTI-PROJECT WAFER SERVICE (MPW)

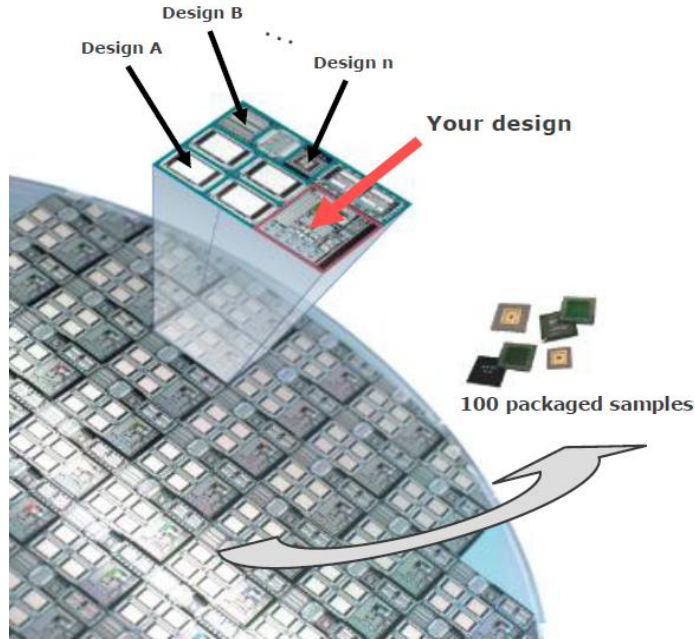

**Reference to a MPW wafer, please verify the current commercial offer.*

- Access to low cost prototyping runs through MPW service
- Mask and wafer fabrication costs are shared between customers
- Small NRE costs
- Extensive check on all submitted designs
- Limit on max number of wafers processed


Contact: ganmpw@imec-int.com

<https://www.imec-int.com/en/innovation/build-your-gan-ics-with-imec-s-gan-on-soi-mpw-process>

<http://europactice-ic.com/mpw-prototyping/power-electronics/>

TECHNOLOGY ACCESS (LOW VOLUME PRODUCTION)

- DEDICATED RUNS

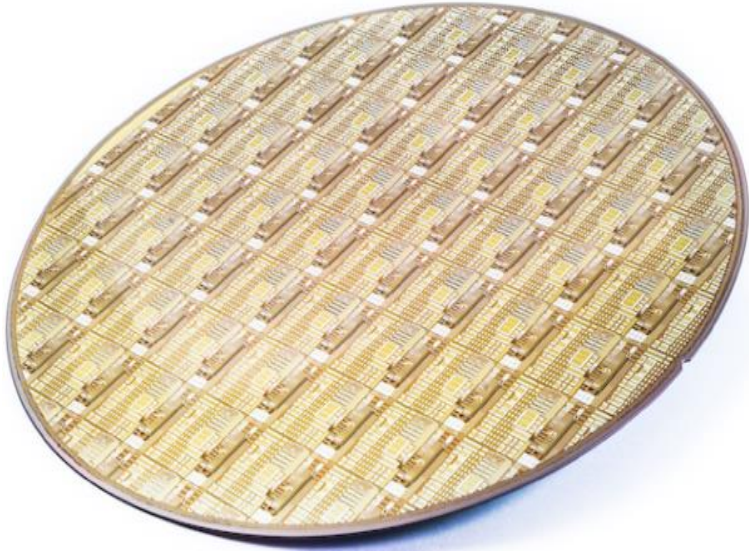

- Dedicated mask runs which return approximately 12 x 200 mm/8 inch wafers. Prices on request
- For even larger production runs, we offer the possibility of engaging with external manufacturing partners

Contact: ganmpw@imec-int.com

<https://www.imec-int.com/en/innovation/build-your-gan-ics-with-imec-s-gan-on-soi-mpw-process>
<http://europractice-ic.com/mpw-prototyping/power-electronics/>